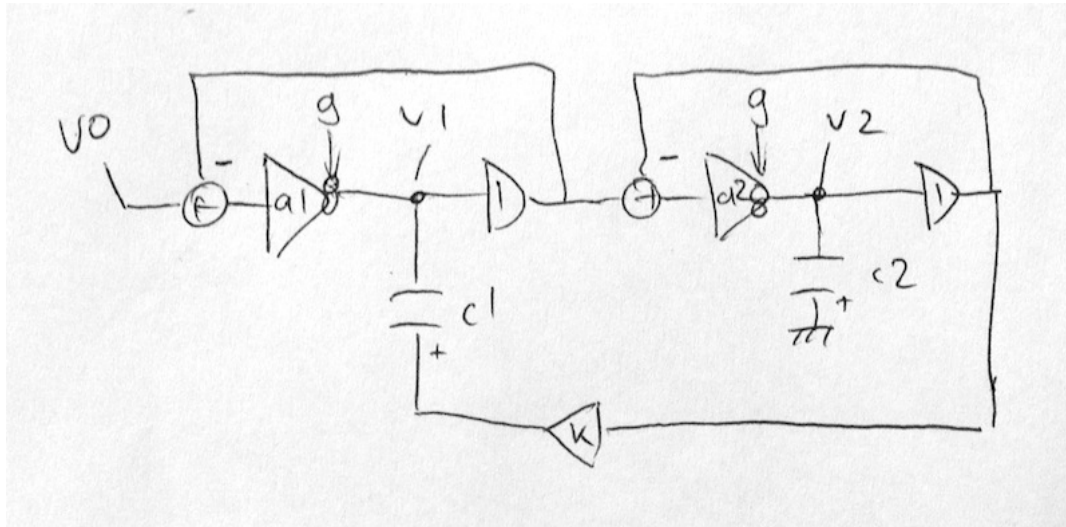


Solving the continuous Sallen Key low pass equations using trapezoidal integration and equivalent currents



References

<http://en.wikipedia.org/wiki/Capacitor>
http://en.wikipedia.org/wiki/Trapezoidal_rule
http://en.wikipedia.org/wiki/Nodal_analysis
<http://qucs.sourceforge.net/tech/node26.html>
<http://www.ecircuitcenter.com/SPICTopics.htm>

Trapezoidal integration of capacitor

$$v_c^{n+1} = v_c^n + \frac{h}{C} \left(\frac{1}{2} i_c^{n+1} + \frac{1}{2} i_c^n \right)$$

$$\frac{2C}{h} v_c^{n+1} - \frac{2C}{h} v_c^n = i_c^{n+1} + i_c^n$$

$$i_c^{n+1} = \frac{2C}{h} v_c^{n+1} - \frac{2C}{h} v_c^n - i_c^n$$

let

$$g_c = \frac{2C}{h}, \quad i_{ceq}^n = g_c v_c^n + i_c^n$$

then

$$i_c^{n+1} = g_c v_c^{n+1} - i_{ceq}^n$$

to update i_{ceq}^{n+1} for the next time step after you have solved for v_c^{n+1} and so i_c^{n+1}

$$i_{ceq}^{n+1} = g_c v_c^{n+1} + i_c^{n+1}$$

$$i_{ceq}^{n+1} = g_c v_c^{n+1} + g_c v_c^{n+1} - i_{ceq}^n$$

so

$$i_{ceq}^{n+1} = 2 g_c v_c^{n+1} - i_{ceq}^n$$

■ Solving for terms using nodal analysis (also called KCL, ie the sum of currents at each node is zero)

```
Clear["Global`*"];
nodev1 = g (v0 - v1) - (gc (v1 - k v2) - ic1eq) == 0
nodev2 = g (v1 - v2) - (gc (v2 - 0) - ic2eq) == 0
subst = {gc -> 1}

Solve[{nodev1, nodev2} /. subst, {v1, v2}, {}][[1]] // FullSimplify
Solve[{nodev1, nodev2} /. subst, {v2}, {v0}][[1]] // FullSimplify

ic1eq + g (v0 - v1) - gc (v1 - k v2) == 0

ic2eq + g (v1 - v2) - gc v2 == 0

{gc -> 1}

{v1 ->  $\frac{ic2eq k + (1 + g) (ic1eq + g v0)}{(1 + g)^2 - g k}$ , v2 ->  $\frac{ic2eq + g (ic1eq + ic2eq + g v0)}{(1 + g)^2 - g k}$ }

{v2 ->  $\frac{ic2eq + g v1}{1 + g}$ }
```

■ Regrouping terms in bounded form

```
FullSimplify[

$$\frac{ic2eq k + (1 + g) (ic1eq + g v0)}{(1 + g)^2 - g k} - \left( \frac{k}{(1 + g)^2 - g k} ic2eq + \frac{(1 + g)}{(1 + g)^2 - g k} ic1eq + \frac{(1 + g) g}{(1 + g)^2 - g k} v0 \right)$$

FullSimplify[ $\frac{ic2eq + g (ic1eq + ic2eq + g v0)}{(1 + g)^2 - g k} -$ 


$$\left( \frac{(1 + g)}{(1 + g)^2 - g k} ic2eq + \frac{g}{(1 + g)^2 - g k} ic1eq + \frac{g^2}{(1 + g)^2 - g k} v0 \right)]$$

0
0
```

■ Plotting regrouped terms

```
a0 = 1 / ((1 + g)^2 - g k) /. {g -> Tan[π wc]};
a1 = k a0 /. {g -> Tan[π wc]};
a2 = (1 + g) a0 /. {g -> Tan[π wc]};
a3 = g a2 /. {g -> Tan[π wc]};
a4 = g a0 /. {g -> Tan[π wc]};
a5 = g a4 /. {g -> Tan[π wc]};

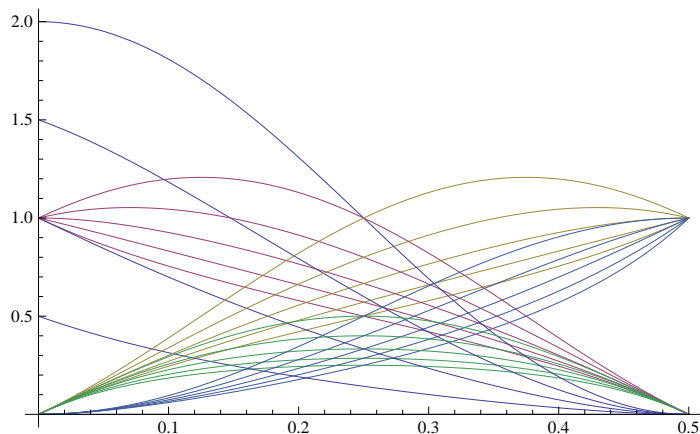Show[
Table[Plot[{a1, a2, a3, a4, a5}, {wc, 0, 1/2}, PlotRange -> All], {k, 0, 2, 0.5}]]
```



Final algorithm

```

Clear
icleq = 0;
ic2eq = 0;

Set
g = Tan[ $\pi$  cutoff/samplerate];
k = 2*res;
a0 = 1/((1+g)2 - g k);
a1 = k*a0;
a2 = (1 + g)*a0;
a3 = g*a2;
a4 = g*a0;
a5 = g*a4;

Tick
(9*, 7+ , 16 total ops for low)

v1 = a1*ic2eq + a2*icleq + a3*v0;
v2 = a2*ic2eq + a4*icleq + a5*v0;
icleq = 2*(v1 - k*v2) - icleq;
ic2eq = 2*(v2          ) - ic2eq;

low = v2

```

Final algorithm using v1 to compute v2

```

Clear
icleq = 0;
ic2eq = 0;

Set
g = Tan[ $\pi$  cutoff/samplerate];
k = 2*res;
a0 = 1/((1+g)2 - g k);
a1 = k*a0;
a2 = (1 + g)*a0;
a3 = g*a2;
a4 = 1/(1 + g);
a5 = g*a4;

Tick
(8*, 6+ , 14 total ops for low)

v1 = a1*ic2eq + a2*icleq + a3*v0;
v2 = a4*ic2eq + a5*v1;
icleq = 2*(v1 - k*v2) - icleq;
ic2eq = 2*(v2          ) - ic2eq;

low = v2

```

Test of algorithm

```

ClearState[] := Block[{},
  ic1eq = 0;
  ic2eq = 0;
];

SetCoeff[cutoff_, res_, samplerate_] := Block[{},
  g = Tan[ $\pi$  cutoff / samplerate];
  k = 2 * res;
  a0 = 1 / ((1 + g)2 - g k);
  a1 = k * a0;
  a2 = (1 + g) * a0;
  a3 = g * a2;
  a4 = g * a0;
  a5 = g * a4;
];

Tick[t_, v0_] := Block[{v1, v2, v3},
  v1 = a1 * ic2eq + a2 * ic1eq + a3 * v0;
  v2 = a2 * ic2eq + a4 * ic1eq + a5 * v0;
  ic1eq = 2 * (v1 - k * v2) - ic1eq;
  ic2eq = 2 * (v2) - ic2eq;
  Return[{t, v0, v2}]
];

h = 1.0 / 44100.0;
t1 = 0.005;
drive = 1;
freq = 1000.0;

MySaw[x_] := 2 (x - Floor[x] - 0.5);
MyOsc[x_] := drive MySaw[freq x];

ClearState[];
SetCoeff[500.0, 0.5, 44100.0];
tp0 = Table[Tick[t, MyOsc[t]], {t, 0, t1, h}];

ListPlot[{tp0[[All, {1, 2}]]}, PlotLabel -> "input", Joined -> True, PlotRange -> All]
ListPlot[{tp0[[All, {1, 3}]]}, PlotLabel -> "low", Joined -> True, PlotRange -> All]

```

